

NAME: Soumyajit Bhowmik

Student ID: 231001003010

Batch:- BEE2

1. Explain the basic logic gate expression (AND, OR, NOT, NAND, NOR, XOR) with truth tables and logic gate symbols, Design a logic gate circuit using only NAND gates to implement an XOR function.

Ans:- AND Gate:-

Symbol:  $\Rightarrow$

Expression:  $A \cdot B = Y$

Truth Table:

A	B	output
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate:-

Symbol:  $\Rightarrow$

Expression:  $A + B = Y$

Truth Table:-

A	B	output
0	0	0
1	0	1
0	1	1
1	1	1

NOT Gate:-

Symbol:  $\Rightarrow$

Expression:  $\bar{A} = Y$

Truth Table:-

A	output
0	1
1	0

## NAND Gate:-

Symbol:  $\Rightarrow \text{D}$

Expression:  $\overline{A \cdot B} = Y$

Truth Table:

A	B	output
0	0	1
0	1	1
1	0	1
1	1	0

## NOR Gate:-

Symbol:  $\Rightarrow \text{D}$

Expression:  $\overline{A + B} = Y$

Truth Table:-

A	B	output
0	0	1
0	1	0
1	0	0
1	1	0

## XOR Gate:-


Symbol:  $\Rightarrow \text{D}$

Expression:  $(A \cdot \bar{B}) + (\bar{A} \cdot B)$

Truth Table:-

A	B	output
0	0	0
1	0	1
0	1	1
1	1	0

## XOR using NAND:-

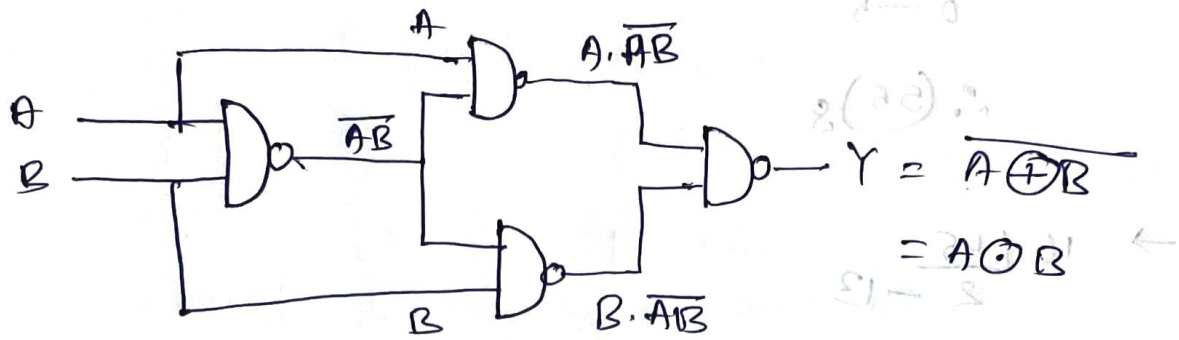

## Truth Table:-

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

2. Convert the following decimal numbers to binary, octal and hexadecimal

i) 45

ii) 255

Also perform 8-bit 2's complement subtraction of 45-100 in binary.

Ans:- i)  $(45)_{10} \rightarrow (?)_2$   
Dividing by 2

$$\begin{array}{r} 2 \overline{) 45} \\ 2 \overline{) 22} \quad -1 \\ 2 \overline{) 11} \quad -0 \\ 2 \overline{) 5} \quad -1 \\ 2 \overline{) 2} \quad -1 \\ 1 \quad -0 \end{array}$$


$$\therefore (101101)_2$$

$$\rightarrow \begin{array}{r} 8 \overline{) 45} \\ 8 \overline{) 5} - 5 \\ 0 - 5 \end{array}$$

$$\therefore (55)_8$$

$$\rightarrow \begin{array}{r} 16 \overline{) 45} \\ 2 - 13 \end{array}$$

$$\therefore (2D)_{16}$$

 

$$ii) (255)_{10} \rightarrow (?)_2$$

$$\begin{array}{r} 2 \overline{) 255} \\ 2 \overline{) 127} - 1 \\ 2 \overline{) 63} - 1 \\ 2 \overline{) 31} - 1 \\ 2 \overline{) 15} - 1 \\ 2 \overline{) 7} - 1 \\ 2 \overline{) 3} - 1 \\ 1 - 1 \end{array}$$

Y	Z
0	0
1	1
1	0
0	1

$$\therefore (11111111)_2$$

$$\rightarrow \begin{array}{r} 8 \overline{) 255} \\ 8 \overline{) 31} - 7 \\ 3 - 7 \end{array}$$

$$\therefore (377)_8$$

$$\rightarrow \begin{array}{r} \cancel{18 \overline{) 255}} \quad 16 \overline{) 255} \\ 15 - 15 \end{array}$$

$$\therefore (15F)_{16}$$



Now, 45 in decimal  $00101101$   
 100 in decimal  $01100100$

1's complement  $100 \rightarrow 10011011$   
 For 2's Complement  $\rightarrow 10011011$   
 $+ 1$   
 $\hline 10011100$

Now, adding 2's complement 100 & 45

$00101101$   
 $+ 10011100$   
 $\hline 11001001 \rightarrow \text{result}$

The result  $11001001$  is in 2's complement form, since the MSB is 1, the number is negative.

Now, 1's complement of result  $00110110$  & adding 1 to it

we get,  $00110110$   
 $+ 1$   
 $\hline 00110111$

which is decimal of 55

Thus, the final value is  $\boxed{-55}$ . Ans

3. Differentiate between TTL, Schottky TTL, and CMOS logic families in terms of speed, power, consumption and fan-out. Also explain how CMOS and TTL families can be interfaced.

Ans:

Parameters	TTL	Schottky TTL	CMOS
$\rightarrow$ Speed	Moderate (1050ns delay)	High (310ns) delay	Very High (0.010)ns
$\rightarrow$ Power Consumption	High (mW range)	Lower than TTL	Very Low ( $\mu$ W range)
$\rightarrow$ Fan-out	~10	~1020	very high (>50)

To interface CMOS and TTL logic families, consider the following method:-


1) CMOS to TTL interface:- When both device operates at same 5V supply, a CMOS output can drive a TTL input directly. However, if the CMOS operates at higher voltage, a level shifter or CMOS buffer is recommended to ensure voltage compatibility.

2) TTL to CMOS:- TTL outputs may not meet the voltage levels required for CMOS inputs. A common solution is to use a pull-up resistor to raise the TTL output to a sufficient voltage of CMOS inputs. Alternatively, an open-collector TTL buffer can be used to interface with CMOS.

These techniques ensure proper voltage and current levels facilitating reliable communication between CMOS & TTL devices.

 4. Simplify the boolean function  $F(A, B, C, D) = \sum(1, 3, 7, 11, 15)$  using a 4 variable Karnaugh map. Implement the simplified expression using basic gates.


Ans:- Since, the highest value of  $F(A, B, C, D) = \sum(1, 3, 7, 11, 15)$  is 15, we are going to choose a 4x4 map {following ESOP}



Nomenclature of Group 1  $\rightarrow \bar{A}\bar{B}D$   
 Nomenclature of Group 2  $\rightarrow CD$

$$\therefore F = \bar{A}\bar{B}D + CD$$

$$Y = (\bar{A}\bar{B} + C)D$$

 

5) Design a 4:1 multiplexer using logic gates. Use the multiplexer to implement the function  $F(A, B) = A \oplus B$

Ans:

$$S_0 S_1 = 00, Y = I_0$$

$$S_0 S_1 = 01, Y = I_1$$

$$S_1 S_0 = 10, Y = I_2$$

$$S_1 S_0 = 11, Y = I_3$$

$$\therefore A \oplus B$$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Mapping XOR to 4:1 Mux inputs.

$$I_0 = 0 (A=0, B=0)$$

$$I_1 = 1 (A=0, B=1)$$

$$I_2 = 1 (A=1, B=0)$$

$$I_3 = 0 (A=1, B=1)$$



Now, selecting inputs using select lines,

$$I_1 = A$$

$$I_0 = B$$

So, i)  $A=0$  and  $B=0$ ,  $S_1 S_0 = 00$

ii)  $A=0$  and  $B=1$ ,  $S_1 S_0 = 01$

iii)  $A=1$  and  $B=0$ ,  $S_1 S_0 = 10$

iv)  $A=1$  and  $B=1$ ,  $S_1 S_0 = 11$

Hence


i)  $Y_1 = I_0 = 0$

ii)  $Y_2 = I_1 = 1$

iii)  $Y_3 = I_2 = 1$

iv)  $Y_4 = I_3 = 0$

which produces desired XOR input.

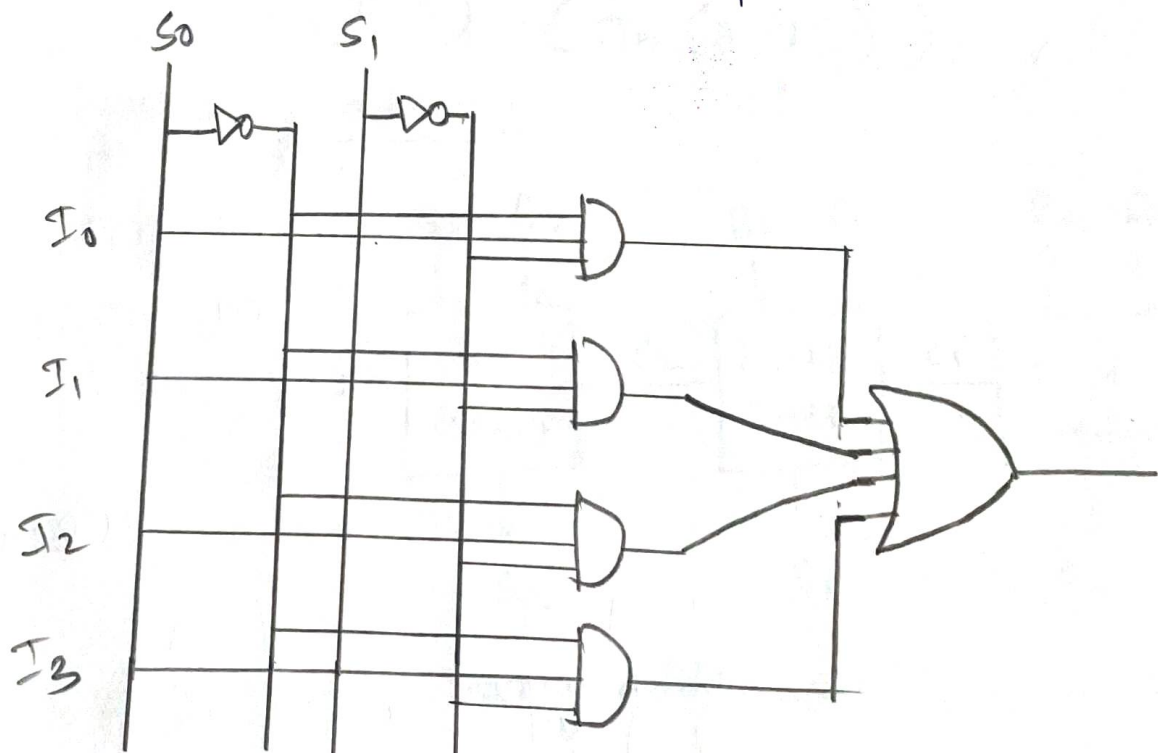



6) Explain the working of a full adder. Design a 4-bit ripple carry adder using full adder circuits. What are its limitations? suggest how a carry look-ahead adder can improve performance.

Ans:- A full adder is a digital circuit that completes the sum of three binary bits: two significant and a carry input. It produces two outputs.

Sum(S): The least significant bit of the addition.


Carry out: The most significant bit, which is carried to the next addition stage.

Boolean equations:-

$$\text{Sum} = (A \oplus B) \oplus C_{in}$$

$$\text{Cout} = (A \cdot B) + (C_{in} (A \oplus B))$$

4-Bit Ripple Carry adder:-

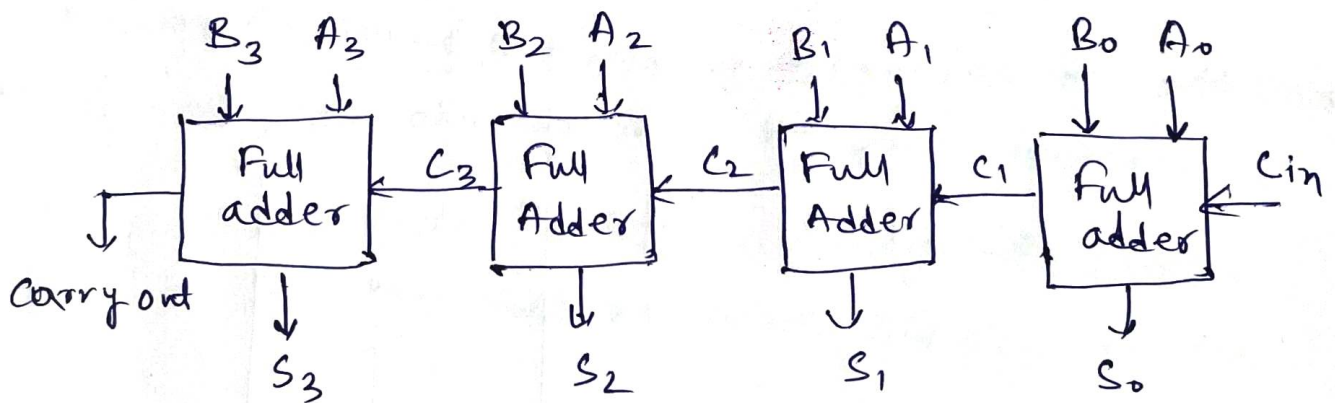

→ Limitation of ripple carry adder:-

i) Propagation delay:- For an  $n$ -bit adder, the delay is proportional to  $n$ . Each <sup>full</sup> adder must wait for the carry from the previous stage leading to a cumulative delay.

ii) Speed:- As the bit-width increases, the delay becomes significant, reducing the overall speed of the addition operation.

iii) Scalability :- Not ideal for large bit-width additions due to ~~in~~ increase delay.

→ Carry look Ahead Adder :- (CLA)

A carry look-ahead adder improves upon the Ripple carry Adder by reducing the carry propagation delay.

Working :-

→ Generate :- Indicates if a carry will be generated at bit position.

→ Propagate :- Indicates if a carry input to bit position will propagate to the next bit.

Advantages :-

→ Reduce delay :- By calculating carries in parallel, the overall delay is significantly reduced.

→ Improved speed :- Enhances the speed of addition operations, specially for large bit width numbers.

7) Design and explain a BCD to 7-segment decoder circuit. What role does a driver IC play in this context?

Ans :- A. BCD to 7-segment decoder is a combination circuit that transforms a 4 bit BCD input representing decimal digit into the signal necessary to create the segments of a 7-segment display displaying the corresponding digit.

Working of BCD to 7-segment decoder :-


BCD input :- The circuit receives a 4 bit BCD input (A, B, C, D), where each bit represents a power of 2 ( $2^3, 2^2, 2^1, 2^0$ )



Truth Table:- A truth table defines the relationship between the BCD input and the 7-segment display segment output - (a, b, c, d, e, f, g)

Logic Gates:-

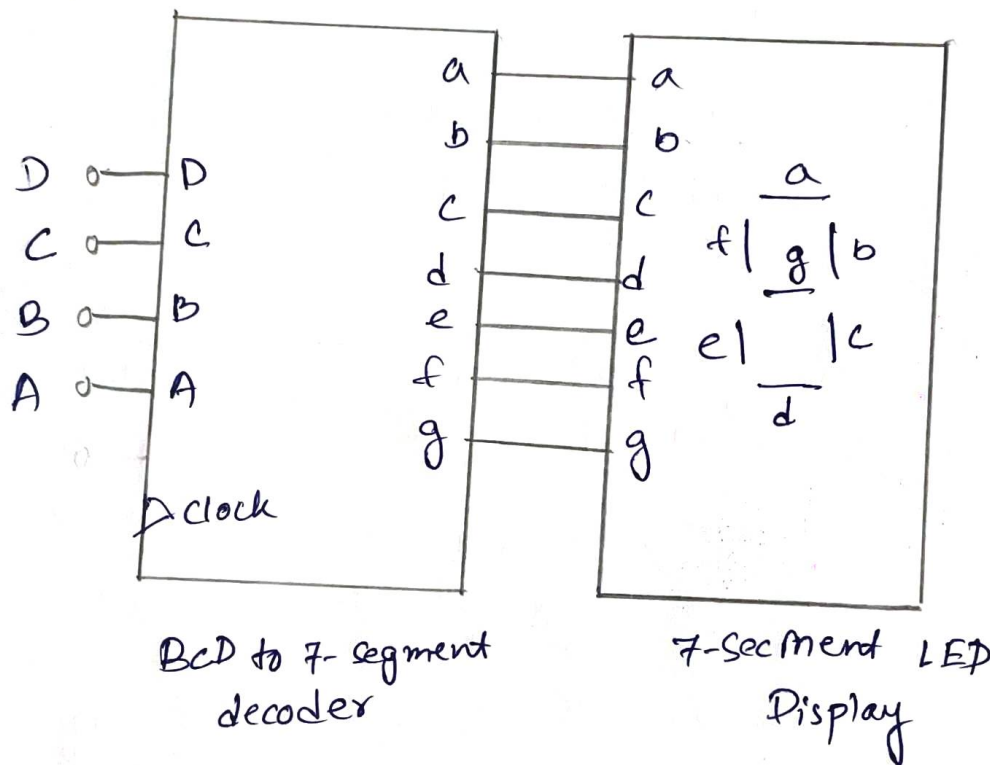The output signals are implemented using logic gates (AND, or NOT) to translate the BCD input into the ~~appropriate~~ appropriate segment activation.



Role of Driver IC in BCD to 7-segment Decoding:-

- 1) Signal conversion:- It converts the 4-bit BCD input to the appropriate signal for the 7-segment display.
- 2) Current ~~and~~ Sinking:- The IC sink current to drive the LED's in the display ensuring illumination display.
- 3) Control features:- Many driver ICs offers additional features like ramp test (LT), blanking and Latch enable (LE) for enhanced control over the display.